Engineering Sector Digital Electronics Design Diploma Eng. Kareem Waseem

# Project 1 Spartan-6 FPGA DSP48A1 Slice

**BY: Youssef Ekramy** 

Under the supervision of:

Eng. Kareem Waseem

# **Table of Contents**

1	DSI	P 48A1 Module	3
	1.1	Code	3
	1.2	Testbench Code	9
	1.3	Do file	.12
	1.4	Waveform	.13
	1.5	Constraint File	.14
	1.6	RTL snippets	.14
	1.7	Elaboration messages	.14
	1.8	Synthesis Schematic	.15
	1.9	Synthesis Messages	.16
	1.10	Synthesis Utilization report	.19
	1.11	Synthesis Timing Report	.20
	1.12	Implementation Schematic	.20
	1.13	Implementation Messages	.20
	1.14	Implementation Utilization Report	.21
	1.15	Implementation Timing Report	22

#### 1 DSP 48A1 Module

#### **1.1** Code

```
module reg mux pipeline #(
    /* This attribute determines if there is register or not
       1 => Registered
                                         (DEFAULT)
        0 => NO Register
    parameter REG = 1,
    /* This attribute determines the width of the inputs */
    parameter WIDTH = 18,
    /* It selects whether all resets asynchronous /synchronous
       "ASYNC" => Asynchronous
       "SYNC" => Synchronous
                                                   (DEFAULT) */
    parameter RSTTYPE = "SYNC"
) (
    input clk, enable, rst,
    input [WIDTH-1:0] in,
    output [WIDTH-1:0] out
);
    generate
        if (REG == 1) begin
            reg [WIDTH-1:0] in r;
            if(RSTTYPE == "ASYNC")
                always @(posedge clk or posedge rst) begin
                    if(rst)
                        in r <= 0;
                    else if(enable)
                        in_r <= in;</pre>
                end
            else if(RSTTYPE == "SYNC")
                always @(posedge clk) begin
                    if(rst)
                         in_r <= 0;
                    else if(enable)
                        in_r <= in;</pre>
                end
            assign out = in_r;
        else
            assign out = in;
    endgenerate
endmodule
```

```
module DSP48A1Module #(
    /* A0 and B0 are the first stages of the pipelines
       A1 and B1 are the second stages of the pipelines */
   parameter AOREG = 0, parameter BOREG = 0, // Default: NO registers
   parameter A1REG = 1, parameter B1REG = 1, // Default: registered
   /* The number defines the number of pipeline stages. */
   parameter CREG = 1, parameter DREG = 1,
   parameter MREG = 1, parameter PREG = 1,
   parameter CARRYINREG = 1, parameter CARRYOUTREG = 1,
   parameter OPMODEREG = 1,
   /* The CARRYINSEL attribute is used in carry cascade input
       "CARRYIN" => the CARRYIN input will be considered
       "OPMODE5" => the value of opcode[5] (DEFAULT)
                 => if none of these string values exist. */
   parameter CARRYINSEL = "OPMODE5",
   /* It defines whether the input to the B port is routed
       "DIRECT" => routed from the B input (DEFAULT)
       "CASCADE" => the cascaded input (BCIN) from the previous DSP48A1 slice
               => if none of these string values exist. */
   parameter B_INPUT = "DIRECT",
   /* It selects whether all resets asynchronous /synchronous
      "ASYNC" => Asynchronous
                                                (DEFAULT) */
   parameter RSTTYPE = "SYNC"
   input [17:0] A, B, D,
   input [47:0] C,
   input CARRYIN,
   output [35:0] M,
   output [47:0] P,
   output CARRYOUT, CARRYOUTF,
   /* Control Input Ports */
   input clk,
   input [7:0] OPMODE,
   /* Clock Enable Input Ports */
   input CEA, CEB, CEC,
   input CED, CEM, CEP,
   input CEOPMODE, CECARRYIN,
   /* Reset Input Ports */
   input RSTA, RSTB, RSTC,
    input RSTD, RSTM, RSTP,
    input RSTOPMODE, RSTCARRYIN,
```

```
/* Cascade Ports */
    input [17:0] BCIN,
    output [17:0] BCOUT,
    input [47:0] PCIN,
    output [47:0] PCOUT
);
   /* First pipeline stage of inputs
    reg [17:0] B0_in; // Handling the input of B0
    always @(*) begin
        case(B_INPUT)
        "DIRECT": B0_in = B;
        "CASCADE": B0 in = BCIN;
        default: B0_in = 0;
        endcase
   wire [17:0] A0_out, B0_out, D_out; // Outputs of first pipeline stage
   wire [47:0] C_out; wire [7:0] OPMODE_out;
    reg_mux_pipeline #(.REG(A0REG),.RSTTYPE(RSTTYPE)) in_A0 (.clk(clk),
                                                             .enable(CEA),
                                                             .rst(RSTA),
                                                             .in(A),
                                                             .out(A0_out));
    reg_mux_pipeline #(.REG(BOREG),.RSTTYPE(RSTTYPE)) in_BO (.clk(clk),
                                                             .enable(CEB),
                                                             .rst(RSTB),
                                                             .in(B0_in),
                                                             .out(B0_out));
    reg_mux_pipeline #(.REG(CREG),.WIDTH(48),.RSTTYPE(RSTTYPE)) in_C (.clk(clk),
                                                                     .enable(CEC),
                                                                     .rst(RSTC),
                                                                     .in(C),
                                                                     .out(C_out));
    reg_mux_pipeline #(.REG(DREG),.RSTTYPE(RSTTYPE)) in_D (.clk(clk),
                                                             .enable(CED),
                                                             .rst(RSTD),
                                                             .in(D),
                                                             .out(D_out));
    reg mux pipeline #(.REG(OPMODEREG),.WIDTH(8),.RSTTYPE(RSTTYPE)) in_OPMODE (.clk(clk),
                                                                                  .enable(CE
OPMODE),
```

```
.rst(RSTOP
MODE),
                                                                                  .in(OPMODE
                                                                                  .out(OPMOD
E_out));
       PRE-ADDER/SUBTRACTOR level*/
   wire [17:0] PRE_ADD_SUB_out;
   assign PRE_ADD_SUB_out = (OPMODE_out[6] == 0)?
                             (D_out + B0_out):
                             (D_out - B0_out);
    /* Second pipeline stage of inputs
        instance name in_(name of Input)
   wire [17:0] B1_in; // Handling the input of B1
   assign B1_in = (OPMODE_out[4] == 0)? B0_out : PRE_ADD_SUB_out;
   wire [17:0] A1_out, B1_out;
   reg_mux_pipeline #(.REG(A1REG),.RSTTYPE(RSTTYPE)) in_A1 (.clk(clk),
                                                             .enable(CEA),
                                                             .rst(RSTA),
                                                             .in(A0_out),
                                                             .out(A1 out));
    reg_mux_pipeline #(.REG(B1REG),.RSTTYPE(RSTTYPE)) in_B1 (.clk(clk),
                                                             .enable(CEB),
                                                             .rst(RSTB),
                                                             .in(B1_in),
                                                             .out(B1_out));
   assign BCOUT = B1_out;
   /* MULTIPLIER level */
   wire [35:0] Multiplier_out;
    assign Multiplier_out = A1_out * B1_out;
   wire [35:0] M_out;
    reg_mux_pipeline #(.REG(MREG),.WIDTH(36),.RSTTYPE(RSTTYPE)) in_M (.clk(clk),
                                                                     .enable(CEM),
                                                                     .rst(RSTM),
                                                                     .in(Multiplier_out),
                                                                     .out(M_out));
   assign M = M_out; //Buffered M Output
   /* MUX X level */
    reg [47:0] X_out;
   wire [47:0] P_out;
```

```
always @(*) begin
        case (OPMODE out[1:0])
            0: X_out = 0; // disable the post-adder/subtracter and propagate the MUX Z
result to P
            1: X out = {{12{1'b0}}, M out}; // Use the multiplier product
            2: X_out = P_out; // Use the P output signal (accumulator)
            3: X_out = {D_out[11:0],A1_out[17:0],B1_out[17:0]}; // Use the concatenated
D:A:B input signals
        endcase
    end
   /* MUX Z level */
    reg [47:0] Z_out;
    always @(*) begin
        case (OPMODE_out[3:2])
            0: Z out = 0; //disable the post-adder/subtracter and propagate the multiplier
product or other X result to P)
           1: Z_out = PCIN;
            2: Z_out = P_out;
            3: Z_out = C_out;
        endcase
    /* CARRYIN POST ADDER/SUBTRACTOR level */
    reg CYI in;
    wire CYI_out;
    always @(*) begin
        case (CARRYINSEL)
            "CARRYIN": CYI_in = CARRYIN;
            "OPMODE5": CYI_in = OPMODE_out[5];
            default: CYI_in = 0;
        endcase
    reg_mux_pipeline #(.REG(CARRYINREG),.WIDTH(1),.RSTTYPE(RSTTYPE)) in_CYI(.clk(clk),
                                                                             .enable(CECARR
YIN),
                                                                             .rst(RSTCARRYI
N),
                                                                             .in(CYI_in),
                                                                              .out(CYI_out))
    /* POST-ADDER/SUBTRACTOR level*/
   wire [47:0] POST_ADD_SUB_out;
   wire CYO_in,CYO_out;
    assign {CYO in,POST ADD SUB out} = (OPMODE out[7] == 0)?
                                        (Z_out + X_out + CYI_out):
                                        (Z_out - (X_out + CYI_out));
    /* P pipeline register */
```

```
reg_mux_pipeline #(.REG(PREG),.WIDTH(48),.RSTTYPE(RSTTYPE)) in_P(.clk(clk),
                                                                      .enable(CEP),
                                                                      .rst(RSTP),
                                                                      .in(POST_ADD_SUB_out),
                                                                      .out(P_out));
    assign P = P_out; assign PCOUT = P_out;
    /* CARRYOUT POST ADDER/SUBTRACTOR level */
    reg_mux_pipeline #(.REG(CARRYOUTREG),.WIDTH(1),.RSTTYPE(RSTTYPE)) in_CYO(.clk(clk),
                                                                              .enable(CECARR
YIN),
                                                                              .rst(RSTCARRYI
N),
                                                                              .in(CYO_in),
                                                                              .out(CYO_out))
    assign CARRYOUT = CYO_out; assign CARRYOUTF =
CYO_out;
endmodule
```

#### 1.2 Testbench Code

```
module DSP48A1Module tb();
   /* Add All the parameters */
   parameter AOREG = 0; parameter BOREG = 0;
   parameter A1REG = 1; parameter B1REG = 1;
   parameter CREG = 1; parameter DREG = 1;
   parameter MREG = 1; parameter PREG = 1;
   parameter CARRYINREG = 1; parameter CARRYOUTREG = 1;
   parameter OPMODEREG = 1;
   parameter CARRYINSEL = "OPMODE5"; parameter B INPUT = "DIRECT";
   parameter RSTTYPE = "SYNC";
   /* Add all the inputs */
   /* Data Ports */
   reg [17:0] A, B, D;
   reg [47:0] C;
   reg CARRYIN;
   wire [35:0] M;
   wire [47:0] P;
   wire CARRYOUT, CARRYOUTF;
   /* Control Input Ports */
   reg clk;
   reg [7:0] OPMODE;
   /* Clock Enable Input Ports */
   reg CEA, CEB, CEC;
   reg CED, CEM, CEP;
   reg CEOPMODE, CECARRYIN;
   /* Reset Input Ports */
   reg RSTA, RSTB, RSTC;
   reg RSTD, RSTM, RSTP;
   reg RSTOPMODE, RSTCARRYIN;
   /* Cascade Ports */
   reg [17:0] BCIN;
   wire [17:0] BCOUT;
   reg [47:0] PCIN;
   wire [47:0] PCOUT;
   /* Self Checker Port*/
   reg [47:0] P_expected;
   /* Instantiate the DUT */
   DSP48A1Module #(.AOREG(AOREG),.A1REG(A1REG),
                    .BOREG(BOREG),.B1REG(B1REG),
                    .CREG(CREG),.DREG(DREG),
```

```
.MREG(MREG),.PREG(PREG),
                .CARRYINREG(CARRYINREG),.CARRYOUTREG(CARRYOUTREG),
               .OPMODEREG(OPMODEREG),
               .CARRYINSEL(CARRYINSEL),.B_INPUT(B_INPUT),
               .RSTTYPE(RSTTYPE))
               DUT (.*);
/* Clock Generation */
initial begin
    clk = 0;
    forever begin
    #5; clk = ~clk;
end
/* DIRECTED and RANDOMIZED TESTBENCH */
initial begin
   $display ("START THE SIMULATION");
   $display ("----");
   /* Initialize Inputs */
   A = 0; B = 0; D = 0; C = 0;
   CARRYIN = 0; OPMODE = 0;
   CEA = 0; CEB = 0; CEC = 0;
   CED = 0; CEM = 0; CEP = 0;
   CEOPMODE = 0; CECARRYIN = 0;
   RSTA = 0; RSTB = 0; RSTC = 0;
   RSTD = 0; RSTM = 0; RSTP = 0;
   RSTOPMODE = 0; RSTCARRYIN = 0;
   BCIN = 0; PCIN = 0;
   repeat(3) @(negedge clk);
   /* Check the reset functionality */
   // Initialize all the inputs by 1
   A = 1; B = 1; D = 1; C = 1;
   CARRYIN = 1; OPMODE = 1;
   CEA = 1; CEB = 1; CEC = 1;
   CED = 1; CEM = 1; CEP = 1;
   CEOPMODE = 1; CECARRYIN = 1;
   // Initialize reset by 1
   RSTA = 1; RSTB = 1; RSTC = 1;
   RSTD = 1; RSTM = 1; RSTP = 1;
   RSTOPMODE = 1; RSTCARRYIN = 1;
   repeat(3) @(negedge clk);
   // Check the reset functionality
   $display ("Reset_functionality TEST");
   self_checker(P,0);
   $display ("----");
```

```
RSTA = 0; RSTB = 0; RSTC = 0;
RSTD = 0; RSTM = 0; RSTP = 0;
RSTOPMODE = 0; RSTCARRYIN = 0;
/* PRE-ADDER output (Addition) */
A = 18'd1;
B = 18'd5;
D = 18'd3;
C = 48'd100;
OPMODE = 8'b0001_0001;
repeat(4) @(negedge clk);
$display("PRE_ADDER_Addition TEST");
self_checker(P,(B + D) * A);
repeat(2) @(negedge clk);
$display ("----");
/* PRE-ADDER output (Subtraction) */
A = 18'd1;
B = 18'd10;
D = 18'd15;
OPMODE = 8'b0101_0001;
repeat(4) @(negedge clk);
$display("PRE_ADDER_Subtraction TEST");
self_checker(P,(D - B));
repeat(2) @(negedge clk);
$display ("----");
/* MULTIPLIER output */
A = 18'd3;
B = 18'd4;
C = 48'd0;
D = 18'd0;
OPMODE = 8'b0000_0001;
repeat(4) @(negedge clk);
$display("MULTIPLIER TEST");
self_checker(P,(A * B));
repeat(2) @(negedge clk);
$display ("----");
/* POST-ADDER output (Addition) */
A = 18'd5;
B = 18'd6;
C = 48'd50;
OPMODE = 8'b0000_1101;
repeat(4) @(negedge clk);
$display("POST_ADDER_Addition TEST");
self_checker(P,((A * B) + C));
repeat(2) @(negedge clk);
$display ("----");
```

```
/* POST-ADDER output (Subtraction) */
       A = 18'd8;
       B = 18'd2;
       D = 18'd0;
       C = 48'd50;
       OPMODE = 8'b1010 1101;
       repeat(4) @(negedge clk);
       $display("POST_ADDER_Subtraction TEST");
       self_checker(P,(C - ((A * B) + OPMODE[5])));
       repeat(2) @(negedge clk);
       $display ("----");
       $display ("END OF SIMULATION");
       $stop;
   /* Self Checking Task */
   task self_checker(input [47:0] out,expected);
       begin
           if(expected != out) begin
               $display("Error: Expected %d, got %d", expected, out);
               $stop;
           else
               $display("Self Checker: Passed");
       end
   endtask
   /* Monitor the inputs and outputs */
   /* initial begin
        $monitor("OPMODE = %b,A = %d,B = %d, C = %d, D = %d, P = %d",
endmodule
```

## 1.3 Do file

```
vlib work


vlog DSP48A1Module.v DSP48A1Module_tb.v


vsim -voptargs=+acc work.DSP48A1Module_tb

# add Internal signals
add wave DUT/*

run -all
```

## 1.4 Waveform

 


 

#### 1.5 Constraint File

```
## Clock signal
# w5 PIN CONNECTED TO CLOCK 33 IS THE DEFNITION OF 3.3v PASSED TO PINS
set_property -dict {PACKAGE_PIN W5 IOSTANDARD LVCMOS33} [get_ports clk]
#add The name of clock in design after -name
create_clock -period 10.00 -name clk -waveform {0.000 5.000} -add [get_ports clk]
```


## 1.6 RTL snippets

 

## 1.7 Elaboration messages



## 1.8 Synthesis Schematic

 

## 1.9 Synthesis Messages

Enable and rst of reg\_mux\_pipeline design for A0,B0 as they are connected to the input directly without creating a
register due to parameters

```
parameter AOREG = 0, parameter BOREG = 0, // Default: NO registers
```

- o CARRYIN are unconnected by design due to the parameter of { parameter CARRYINSEL = "OPMODE5"} once it changes to "CARRYIN", They will be connected to them.
- O BCIN are unconnected by design due to the parameter of { parameter B\_INPUT = "DIRECT" } once it changes to "CASCADE", They will be connected to them.

Name	Severity	Details
Vivado_Tcl 4- 321	Status	Starting synth_design
Common 17- 347	Status	Attempting to get a license for feature 'Synthesis' and/or device 'xc7a200t'
Project 1-262	Status	Processing XDC Constraints
Project 1-569	Status	Initializing timing engine
Designutils 20- 179	Status	Parsing XDC File [F:/Electronics/Digital Electronics - KW/Mini_project_DSP48A1/DSP_CONSTRAINT_FILE.xdc]
Designutils 20- 178	Status	Finished Parsing XDC File [F:/Electronics/Digital Electronics - KW/Mini_project_DSP48A1/DSP_CONSTRAINT_FILE.xdc]
Project 1-263	Status	Completed Processing XDC Constraints
Vivado_Tcl 4- 41	Status	29 Infos, 41 Warnings, 0 Critical Warnings and 0 Errors encountered.
Vivado_Tcl 4- 42	Status	synth_design completed successfully
#UNDEF	Status	report_utilization: Time (s): cpu = $00:00:00$ ; elapsed = $00:00:00.082$ . Memory (MB): peak = $906.184$ ; gain = $0.000$
Common 17- 349	Information	Got license for feature 'Synthesis' and/or device 'xc7a200t'
Synth 8-6157	Information	synthesizing module 'reg_mux_pipeline'
Synth 8-6157	Information	synthesizing module 'reg_mux_pipelineparameterized0'
Synth 8-6157	Information	synthesizing module 'reg_mux_pipelineparameterized1'
Synth 8-6157	Information	synthesizing module 'reg_mux_pipelineparameterized2'
Synth 8-6157	Information	synthesizing module 'reg_mux_pipelineparameterized3'
Synth 8-6157	Information	synthesizing module 'reg_mux_pipelineparameterized4'
Synth 8-6155	Information	done synthesizing module 'reg_mux_pipelineparameterized0' (1#1)
Synth 8-6155	Information	done synthesizing module 'reg_mux_pipelineparameterized1' (1#1)
Synth 8-6155	Information	done synthesizing module 'reg_mux_pipelineparameterized2' (1#1)
Synth 8-6155	Information	done synthesizing module 'reg_mux_pipelineparameterized3' (1#1)
Synth 8-6155	Information	done synthesizing module 'reg_mux_pipelineparameterized4' (1#1)
Synth 8-6155	Information	done synthesizing module 'DSP48A1Module' (2#1)
Synth 8-3331	Warning	design reg_mux_pipeline has unconnected port enable
Synth 8-3331	Warning	design reg_mux_pipeline has unconnected port rst
Synth 8-3331	Warning	design DSP48A1Module has unconnected port CARRYIN


Project 1-236	Information	Implementation specific constraints were found while reading constraint file [F:/Electronics/Digital Electronics - KW/Mini_project_DSP48A1/DSP_CONSTRAINT_FILE.xdc]. These constraints will be ignored for synthesis but will be used in implementation. Impacted constraints are listed in the file [.Xil/DSP48A1Module_propImpl.xdc].
<b>Device 21-403</b>	Information	Loading part xc7a200tffg1156-3
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[0]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[1]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[2]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[3]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[4]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[5]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[6]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[7]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[8]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[9]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[10]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[11]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[12]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[13]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[14]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[15]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[16]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[17]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port CARRYIN
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[0]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[1]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[2]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[3]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[4]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[5]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[6]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[7]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[8]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[9]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[10]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[11]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[12]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[13]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[14]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[15]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[17]
Synth 8-3331	Warning	design DSP48A1Module has unconnected port BCIN[17]

		Resolution: To avoid this warning, move constraints listed in ['Undefined'] to another XDC file and exclude this new file from synthesis with the used_in_synthesis property (File Properties dialog in GUI) and re-run elaboration/synthesis.
Synth 8-5818	Information	HDL ADVISOR - The operator resource <adder> is shared. To prevent sharing consider applying a KEEP on the output of the operator</adder>
Synth 8-5842	Information	Cannot pack DSP OPMODE registers because of constant '1' value. Packing the registers will cause simulation mismatch at initial cycle
Project 1-571	Information	Translating synthesized netlist
Netlist 29-17	Information	Analyzing 207 Unisim elements for replacement
Netlist 29-28	Information	Unisim Transformation completed in 0 CPU seconds
Project 1-570	Information	Preparing netlist for logic optimization
Opt 31-138	Information	Pushed 0 inverter(s) to 0 load pin(s).
Project 1-111	Information	Unisim Transformation Summary: No Unisim elements were transformed.
<b>Common 17-83</b>	Information	Releasing license: Synthesis
Constraints 18-5210	Warning	No constraint will be written out.
Common 17- 1381	Information	The checkpoint 'F:/Electronics/Digital Electronics - KW/Mini_project_DSP48A1/DSP48A1/DSP48A1.runs/synth_1/DSP48A1Module.dcp' has been generated.
runtcl-4	Information	Executing : report_utilization -file DSP48A1Module_utilization_synth.rpt -pb DSP48A1Module_utilization_synth.pb
Common 17- 206	Information	Exiting Vivado at Sun Jul 28 02:59:45 2024


## 1.10 Synthesis Utilization report

Name	Slice LUTs (134600)	Slice Registers (269200)	DSPs (740)	Bonded IOB (500)	BUFGCTRL (32)
∨ N DSP48A1Module	230	160	1	327	1
In_P (reg_mux_pipelin	0	48	0	0	0
In_OPMODE (reg_mux	228	8	0	0	0
<b>I</b> in_M (reg_mux_pipelin	0	0	1	0	0
In_D (reg_mux_pipelin	0	18	0	0	0
I in_CYO (reg_mux_pip	0	1	0	0	0
In_CYI (reg_mux_pipel	1	1	0	0	0
In_C (reg_mux_pipelin	0	48	0	0	0
In_B1 (reg_mux_pipeli	0	18	0	0	0
<b>I</b> in_A1 (reg_mux_pipeli	0	18	0	0	0


Resource	Utilization	Available	Utilization %
LUT	230	134600	0.17
FF	160	269200	0.06
DSP	1	740	0.14
IO	327	500	65.40

 


## 1.11 Synthesis Timing Report

 

## 1.12 Implementation Schematic

 

#### 1.13 Implementation Messages

 


## 1.14 Implementation Utilization Report

Name 1	Slice LUTs (133800)	Slice Registers (267600)	Slice (3345 0)	LUT as Logic (133800)	LUT Flip Flop Pairs (133800)	DSP s (740 )	Bonded IOB (500)	BUFGCTRL (32)
∨ N DSP48A1Module	229	179	98	229	50	1	327	1
I in_A1 (reg_mux_pipeli	0	18	6	0	0	0	0	0
In_B1 (reg_mux_pipeli	0	36	10	0	0	0	0	0
In_C (reg_mux_pipelin	0	48	14	0	0	0	0	0
In_CYI (reg_mux_pipel	1	1	1	1	1	0	0	0
In_CYO (reg_mux_pip	0	2	2	0	0	0	0	0
In_D (reg_mux_pipelin	0	18	10	0	0	0	0	0
In_M (reg_mux_pipelin	0	0	0	0	0	1	0	0
In_OPMODE (reg_mux	228	8	75	228	0	0	0	0
In_P (reg_mux_pipelin	0	48	12	0	0	0	0	0

## Summary

Resource	Utilization	Available	Utilization %
LUT	229	133800	0.17
FF	179	267600	0.07
DSP	1	740	0.14
IO	327	500	65.40

 

# 1.15 Implementation Timing Report

#### **Design Timing Summary**

tup		Hold		Pulse Width		
Worst Negative Slack (WNS):	3.858 ns	Worst Hold Slack (WHS):	0.273 ns	Worst Pulse Width Slack (WPWS):	4.500 ns	
Total Negative Slack (TNS):	0.000 ns	Total Hold Slack (THS):	0.000 ns	Total Pulse Width Negative Slack (TPWS):	0.000 ns	
Number of Failing Endpoints:	0	Number of Failing Endpoints:	0	Number of Failing Endpoints:	0	
Total Number of Endpoints:	106	Total Number of Endpoints:	106	Total Number of Endpoints:	181	